

316124



**Mid Semester Examination 2024**  
**Department of Physics, School of Physical Sciences**  
**DOON UNIVERSITY, DEHRADUN**  
**Integrated M.Sc. Physics IV semester**  
**Course: PHC- 253, Digital Systems and Applications**

**Time allowed – 3 hours**

**Max.Marks-50**

**General Instructions**

- This question paper contains three sections A, B, and C.
- Section A contains 5 question 2 mark each
- Section B Contains 4 question 3 mark each
- Section C contains 2 question 4 mark each.
- Attempt all question.

**Section A**

$6 \times 2 = 12$

1. What is Duty cycle
2. In a digital communication system, why might a demultiplexer be used at the receiving end?
3. Show  $A(\bar{B}+C)$  using NOR gate only
4. Conversion of (.4375) to binary.
5. Conversion of  $(AB6)_{16}$  to decimal equivalent
6. What is Race around Condition in flip flops?

**OR**

Define SR latch.

**Section B**

$6 \times 3 = 18$

7. What is the primary difference between a multiplexer (MUX) and a demultiplexer (DEMUX)? Illustrate your answer with appropriate diagrams.
8. Explain how to calculate the duty cycle of a 555 timer in astable mode and provide the formula.
9. What is the primary difference between an encoder and a decoder? Illustrate your answer with appropriate examples.
10. Find X when  $(429)_{10} = X_{16}$ .

11. What is a binary counter, and how does it work? Illustrate your answer with the design and operation of a 3-bit binary counter.
12. Design an astable 555 timer circuit to generate a square wave with a frequency of 1 kHz and a duty cycle of 60%. Provide the values of the resistors ( $R_A$  and  $R_B$ ) and the capacitor ( $C$ ) used in your design. Show all calculations and explain the steps involved.

**OR**

Describe the difference between a D flip-flop and a JK flip-flop. Provide one typical use case for each type. (Draw truth table)

**Section C**

$4 \times 5 = 20$

13. Minimize the following Boolean function using K map
- (a)  $F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 8, 9, 10, 11)$
- (b)  $F(P, Q, R, S) = \pi(0, 1, 3, 5, 6, 7, 10, 14, 15)$
14. Explain the working principle of a 555 timer in astable mode and explain the formula for the time period, Duty cycle and frequency of oscillation.
15. Explain the working principle of a digital encoder and provide an example of a 4-to-2 binary encoder. Describe the function of a 3-to-8 decoder and provide a truth table illustrating its operation.
16. Compare and contrast synchronous and asynchronous counters. What are the advantages and disadvantages of each type?

**OR**

- (a) State and verify Distributive law.
- (b) Express  $P + Q'R$  in canonical SOP form
- (c) Represent  $(X+Y)(Y+Z)(Z+X)$  using NOR gate only